

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 90978

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY 2025.

Second Semester

Electronics and Communication Engineering

EC 3251 — CIRCUIT ANALYSIS

(Common to : Electronics and Telecommunication Engineering)

(Regulations 2021)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State Kirchhoff's Law.
2. Find the equivalent resistance of circuit with three resistors connected in parallel, each having a resistance value of 2 Ohms.
3. State the conditions for maximum power transfer in DC circuits.
4. State Norton theorem.
5. Define instantaneous power in an AC circuit.
6. A sinusoidal voltage is given by $v(t) = 50 \sin (100\pi t + 30^\circ)$. What are the amplitude, angular frequency, and phase angle of the signal?
7. A source-free RL circuit has $R = 5\Omega$ and $L = 2$ H. Calculate the time constant.
8. What is the voltage across an inductor at $t = 0+$ in a source-free RL circuit?
9. Define a tree in network topology.
10. Two coils have $L_1 = 10$ mH, $L_2 = 20$ mH and mutual inductance $M = 5$ mH. Calculate the coefficient of coupling (k).

PART B — (5 × 13 = 65 marks)

11. (a) Using mesh analysis calculate
- (i) equivalent resistance across the terminal of the supply (7)
 - (ii) total current supplied by the source (3)
 - (iii) power delivered to 5 Ω resistors in the circuit shown in Figure 11 (a) (3)

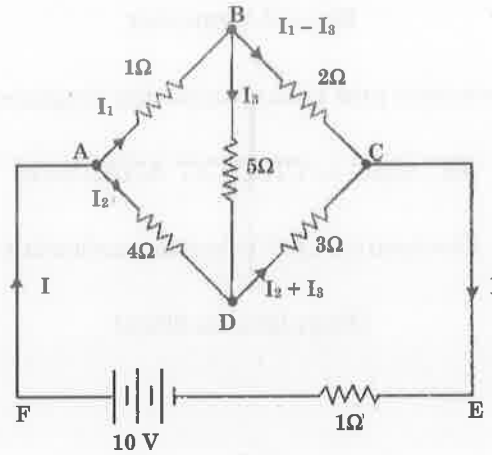


Figure 11 (a)

Or

- (b) (i) A 100 watt, 250 V lamp is connected in series with a 100 watt, 200 V lamp across 250 V supply. Calculate (1) circuit current and (2) voltage across each lamp. Assume the lamp resistances to remain unaltered. (9)
 - (ii) Explain the features and advantages of parallel circuits. (4)
12. (a) Using superposition theorem, Estimate the current in 23 Ω resistor in the circuit shown in Figure. 12 (a)

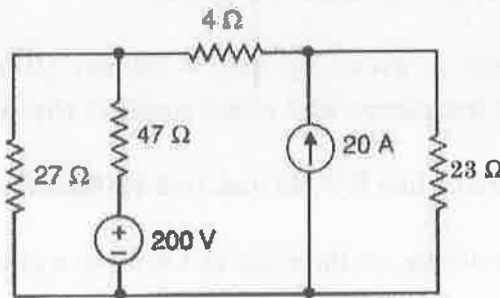


Figure. 12 (a)

Or

- (b) Using Thevenin's theorem, find the current in $10\ \Omega$ resistor in the circuit shown in Figure. 12 (b)

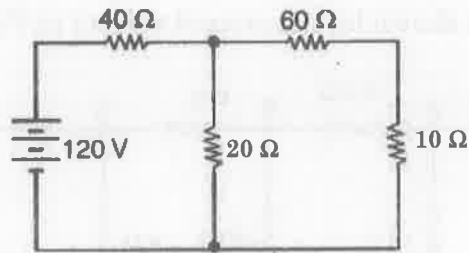


Figure. 12 (b)

13. (a) A coil having a resistance of $7\ \Omega$ and an inductance of $31.8\ \text{mH}$ is connected to $230\ \text{V}$, $50\ \text{Hz}$ supply. Calculate
- the circuit current and phase angle (5)
 - power factor and power consumed and (4)
 - voltage drop across resistor and inductor (4)

Or

- (b) A coil of resistance $50\ \Omega$ and inductance $318\ \text{mH}$ is connected in parallel with a circuit consisting of a $75\ \Omega$ resistor in series with a $159\ \mu\text{F}$ capacitor. The circuit is connected to a $230\ \text{V}$, $50\ \text{Hz}$ supply. Determine the supply current and circuit power factor.

14. (a) Explain the concept of resonance in a series RLC circuit.

Or

- (b) A parallel LC circuit has an inductance $L = 100\ \mu\text{H}$ which has a coil resistance of $12\ \Omega$. The capacitor C is adjustable over the range $200\ \text{pF}$ to $300\ \text{pF}$. Find (i) the maximum and minimum resonance frequencies for the circuit (ii) the Q-factor and (iii) bandwidth of the circuit at the two resonance frequency extremes. (5 + 4 + 4)

15. (a) Coils A and B in a magnetic circuit have 600 and 500 turns respectively. A current of $8\ \text{A}$ in coil A produces a flux of $0.04\ \text{Wb}$. If the coefficient of coupling is 0.2, calculate:

- Self-inductance of coil A, with B open-circuited. (5)
- The average e.m.f. induced in coil B when the flux with it changes from zero to full value in 0.02 second. (4)
- Mutual inductance. (4)

Or

- (b) Explain the concept of magnetically coupled circuits with a detailed derivation of the voltage equations in terms of self-inductance (L_1 , L_2) and mutual inductance (M).

PART C — (1 × 15 = 15 marks)

16. (a) Using nodal analysis, estimate the voltages at nodes A, B and C w.r.t. the reference node shown by the ground symbol in Figure . 16 (a)

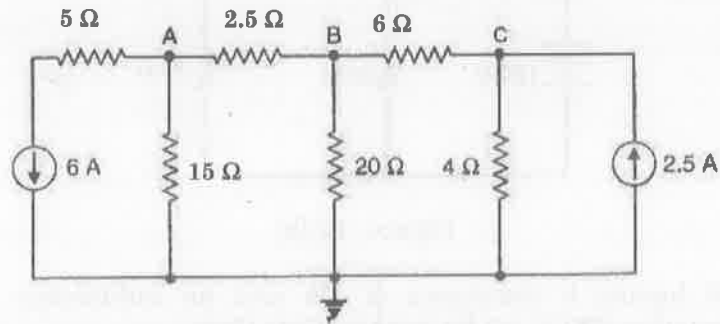


Figure. 16 (a)

Or

- (b) With the help of star/delta transformation, obtain the value of current supplied by the battery in the circuit shown in Figure. 16 (b).

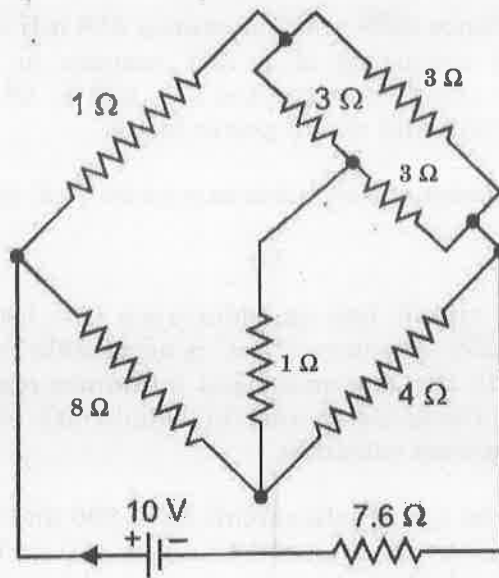


Figure. 16 (b)