

PART B — (5 × 13 = 65 marks)

11. (a) For the circuit shown in Figure 11(a), obtain the equivalent resistance across terminals P and Q.

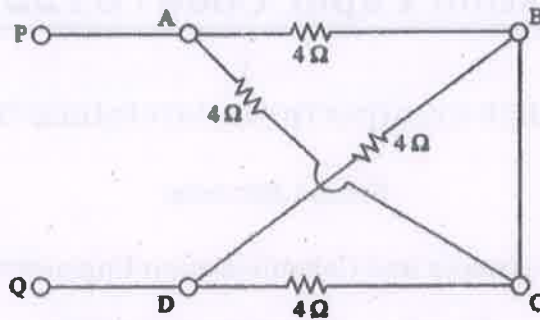


Figure 11(a)

Or

- (b) For the circuit shown in Figure 11(b), find the voltage V_{ab} .

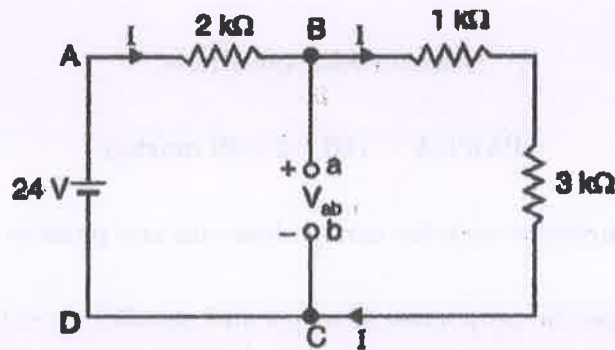


Figure 11(b)

12. (a) For the circuit shown in Figure 12(a), obtain Thevenin's equivalent circuit across terminals ab.

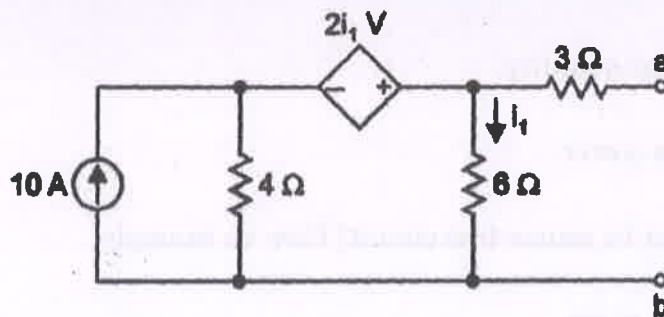


Figure 12(a)

Or

- (b) For the circuit shown in Figure 12 (b), find the current delivered by the source using Delta–Wye conversion

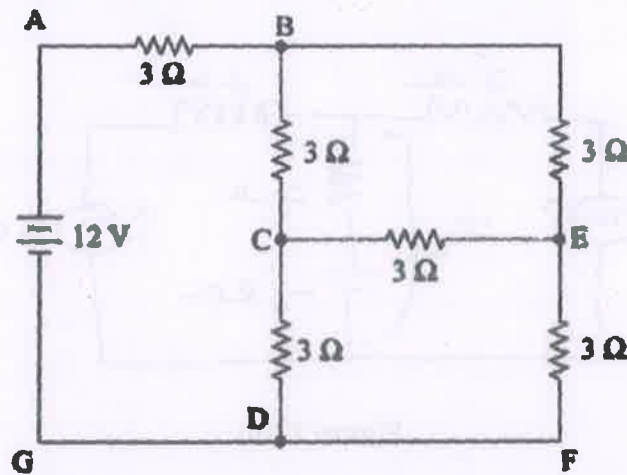


Figure 12(b)

13. (a) An inductive coil of resistance $5\ \Omega$ and inductive reactance $10\ \Omega$ is connected across a voltage of $230\ \text{V}$ at $50\ \text{Hz}$ as shown in Figure 13(a). Calculate the value of the capacitor which when connected in parallel with the coil will bring down the magnitude of the circuit current to a minimum. Draw the phasor diagram.

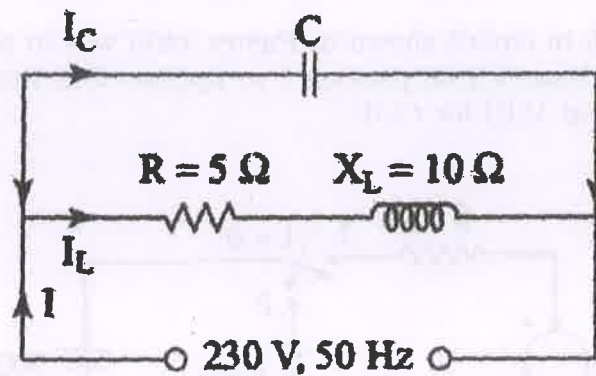


Figure 13(a)

Or

- (b) For the circuit shown in Figure 13(b), find the voltage across load impedance Z_L .

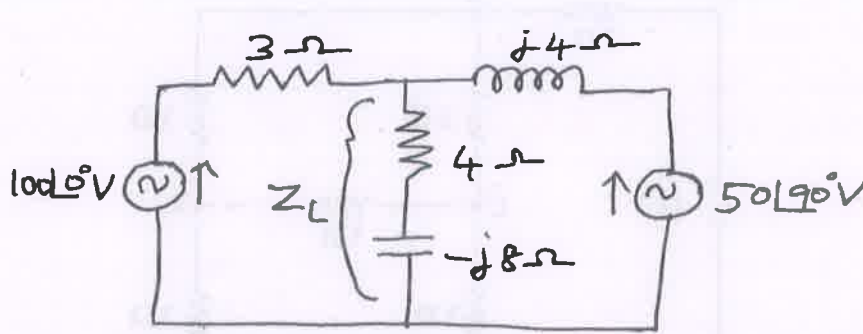


Figure 13(b)

14. (a) An R-L-C series circuit has $R = 10 \Omega$, $L = 0.1 \text{ H}$ and $C = \mu\text{F}$. Calculate the following :
- (i) resonant frequency; (3)
 - (ii) Q-factor of the circuit at resonance; (3)
 - (iii) half-power frequencies and (3)
 - (iv) bandwidth. (4)

Or

- (b) The switch in circuit shown in Figure 14(b) was in position 1 for a long time. It is moved from position 1 to position 2 at time $t = 0$. Sketch the wave form of $V_C(t)$ for $t > 0$.

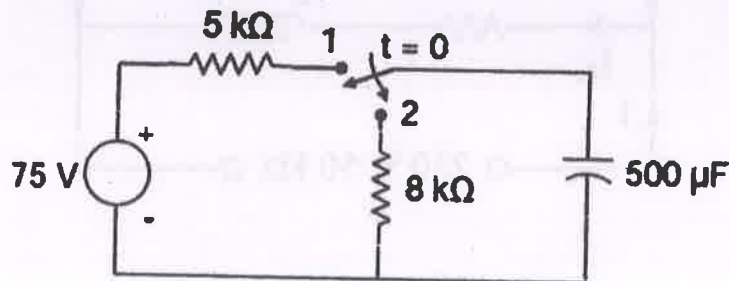


Figure 14(b)

15. (a) For the circuit shown in Figure 15(a), calculate the voltage across $10\ \Omega$ resistor, $V_{10\Omega}$.

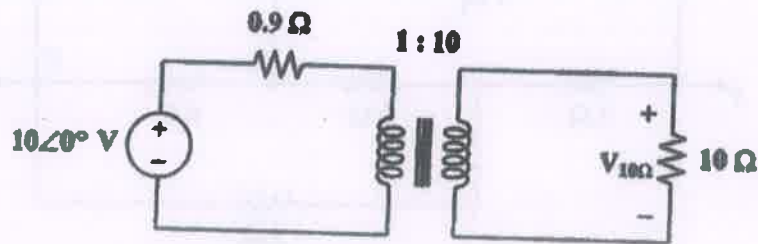


Figure 15(a)

Or

- (b) Explain the procedure for formation of graph, trees and links with an example.

PART C — (1 × 15 = 15 marks)

16. (a) For the circuit shown in Figure 16(a), verify Norton's Theorem by finding the current through the load resistor R_L .

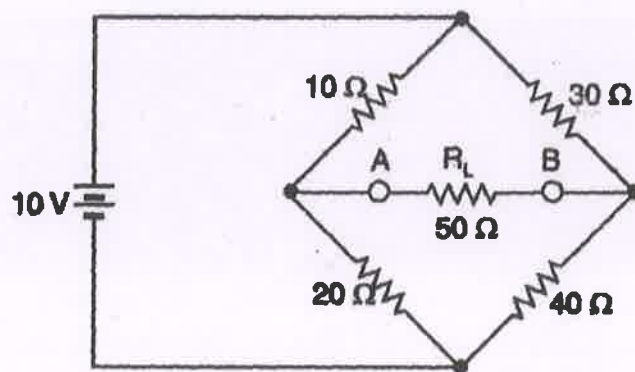


Figure 16(a)

Or

- (b) For the circuit shown in Figure 16(b), Calculate the equivalent resistance of the network across terminals P and Q.

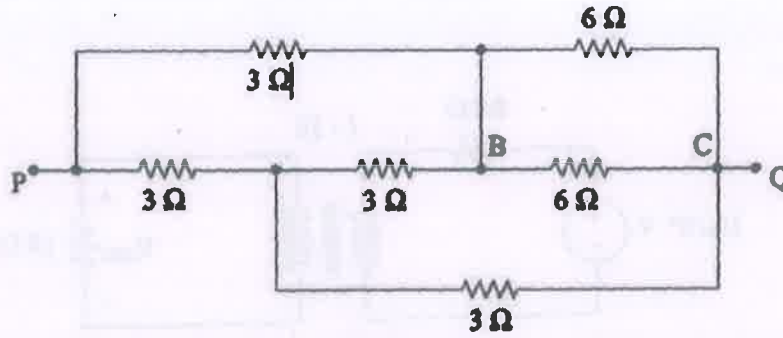


Figure 16(b)

